

MEASURING COAX WITH THE NANO VNA

- LENGTH OR DISTANCE TO FAULT
USING TRANSFORM FUNCTION

- SMITH CHART FUN -

- IMPEDANCE TRANSFORMATION ↗ SWR

- $\frac{1}{4} \lambda$ STUBS

COAX LENGTH USING TRANSFORM

WR2AEW
②

- DISPLAY > TRACE > TRACE 0 ONLY
 - FORMAT = LINEAR OR REAL
- FOR MEASURING LENGTH OR DISTANCE TO FAULT IT IS BEST TO USE:
 - LOW PASS IMPULSE
- TRANSFORM "ON"
- SET VELOCITY FACTOR % (NOT DECIMAL)
- STIMULUS SETTINGS
 - START = 50kHz
 - STOP = (SEE BELOW)
- DISTANCE RANGE & RESOLUTION DETERMINED BY STOP FREQUENCY
 - HIGHER FREQ = SHORTER DISTANCE RANGE
 - LOWER FREQ = LONGER DISTANCE RANGE
- SET STOP BASED ON MAXIMUM EXPECTED DISTANCE

$$\text{STOP FREQ (MHz)} = \frac{5850}{\text{MAX DIST (m)}} \cdot VF$$

(START WITH LOWER FREQ, THEN INCREASE)

INTRODUCTION TO TRANSMISSION LINES ON THE SMITH CHART

- TRANSMISSION LINES ALTER THE IMPEDANCE
WHEN NOT MATCHED

- DUE TO PROPAGATION DELAY
- UGLY MATH!
- EASY ON SMITH CHART



ADDING/REMOVING TRANSMISSION LINE ROTATES
THE IMPEDANCE AROUND THE CENTER

- KEY POINTS:

- COMPLETE TRIP AROUND IS $\frac{1}{2} \lambda$ LONG LINE

- Z REPEATS EVERY $\frac{1}{2} \lambda$ INCREMENT

- HALFWAY AROUND CHART IS $\frac{1}{4} \lambda$ LONG LINE

- Z "INVERTS" $\frac{Z_L}{Z_0} \Rightarrow \frac{Z_0}{Z_L}$

OPEN \Leftrightarrow SHORT

Q: WHEN DOES A 100Ω RESISTOR LOOK LIKE 25Ω ?

A: WHEN IT IS AT THE FAR END OF A $\frac{1}{4}\lambda$ LINE?
(ANY ODD $\frac{1}{4}$ MULTIPLE)

ADDING / REMOVING TRANSMISSION LINE
DOES NOT CHANGE THE SWR

(NOT COUNTING LOSSES)

QUARTER-WAVELENGTH LINES $\frac{\lambda}{4}$

- OFTEN USED IN SWITCH, FILTER, MATCHING, ETC. APPS
- EASY TO MEASURE ON SMITH CHART